



EXAM PAPERS PRACTICE

Boost your performance and confidence with these topic-based exam questions

Practice questions created by actual examiners and assessment experts

Detailed mark scheme

Suitable for all boards

Designed to test your ability and thoroughly prepare you

# 5.1 Current–Voltage Characteristics



XVIII

## PHYSICS

---

# AQA A Level Revision Notes

# A Level Physics AQA

## 5.1 Current-Voltage Characteristics

### CONTENTS

5.1.1 Basics of Electricity

5.1.2 Current-Voltage Characteristics




5.1.1 Basics of Electricity

### Electric Current & Potential Difference

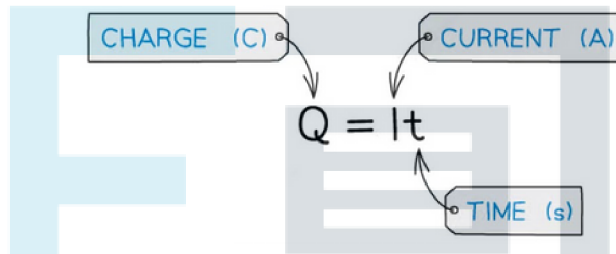
#### Electric Current

- Electric current is defined as **the rate of flow of positive charge** carriers
  - It is measured in units of **amperes (A)** or **amps**
- The charge, current and time are related by the equation:




- Charge is sometimes written as  $\Delta Q$  which means 'change in charge'
  - Similarly, time is written as  $\Delta t$  means 'change in time'
- When two oppositely charged conductors are connected together (by a length of wire), charge will flow between the two conductors, causing a current
- Therefore, rearranging for current,  $I$  gives the equation:

$$I = \frac{\Delta Q}{\Delta t}$$

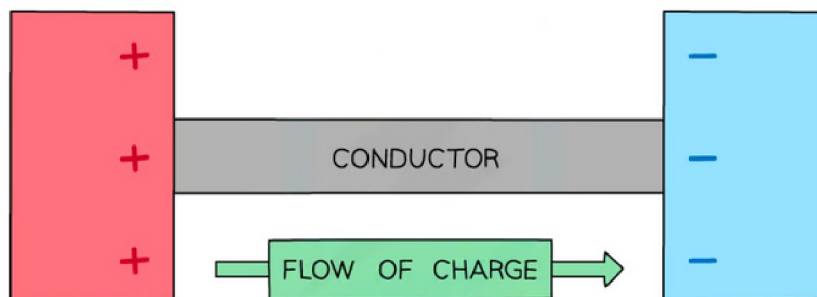

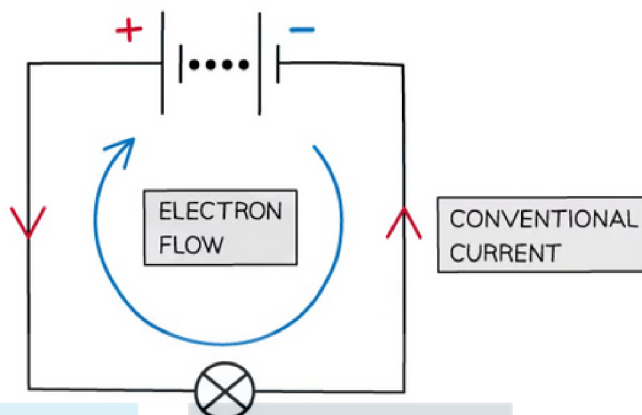
**Charge can flow between two conductors. The direction of conventional current in a metal is from positive to negative**

- In electrical wires, the current is a flow of **electrons**
- Electrons are negatively charged; they flow away from the negative terminal of a cell towards the positive terminal
- Conventional current is defined as the flow of **positive** charge from the **positive terminal of a cell to the negative terminal**
  - This is the opposite to the direction of electron flow, as the conventional current was described before electric current was really understood



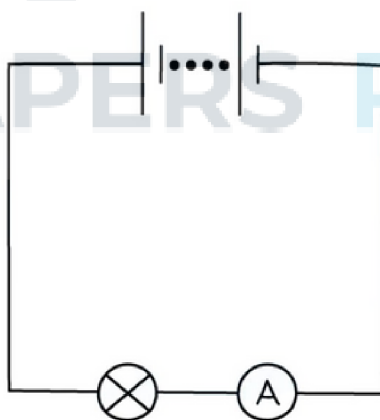**By definition, conventional current always goes from positive to negative (even though electrons go the other way)**

- There are several examples of electric currents, including in household wiring and electrical appliances
- Current is measured using an **ammeter**
- Ammeters should always be connected in **series** with the part of the circuit you wish to measure the current through



**An ammeter can be used to measure the current around a circuit and is always connected in series**


## Potential Difference

- A cell makes one end of the circuit positive and the other negative
- This sets up a **potential difference** across the circuit
  - This is sometimes known as the **voltage**
- The potential difference is defined as **the work done per unit charge** and is measured in units of **volts (V)**

$$V = \frac{W}{Q}$$

POTENTIAL DIFFERENCE (V)      WORK DONE (J)  
 CHARGE (C)

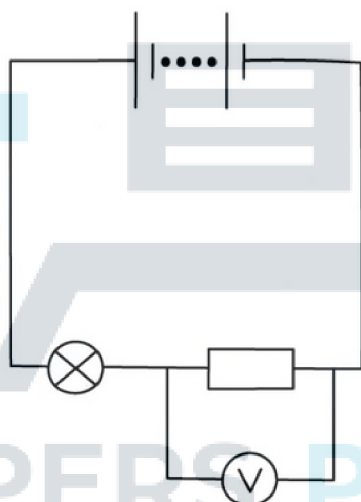- Potential difference (or voltage) is measured using a **voltmeter**
- A voltmeter is always set up in parallel to the component you are measuring the voltage for



**Potential difference can be measured by connecting a voltmeter in parallel between two points in a circuit**

### ? Worked Example

When will 8 mA of current pass through an electrical circuit?

- A. When 1 J of energy is used by 1 C of charge
- B. When a charge of 4 C passes in 500 s
- C. When a charge of 8 C passes in 100 s
- D. When a charge of 1 C passes in 8 s

**ANSWER: B**

**Step 1: Write out the equation relating current, charge and time**

$$Q = It$$

**Step 2: Rule out any obviously incorrect options**

- Option **A** does not contain charge or time, so can be ruled out

**Step 3: Try the rest of the options to determine the correct answer**

- Consider option **B**:

$$I = 4 / 500 = 8 \times 10^{-3} = 8 \text{ mA}$$

- Consider option **C**:

$$I = 8 / 100 = 80 \times 10^{-3} = 80 \text{ mA}$$

- Consider option **D**:

$$I = 1 / 8 = 125 \times 10^{-3} = 125 \text{ mA}$$

- Therefore, the correct answer is **B**




**Exam Tip**

Although electric charge can be positive or negative, since the conventional direction of current is the flow of **positive** charge the current should always be a positive value for your exam answers. Think of potential difference as being the **energy per coulomb** of charge transferred between two points in a circuit
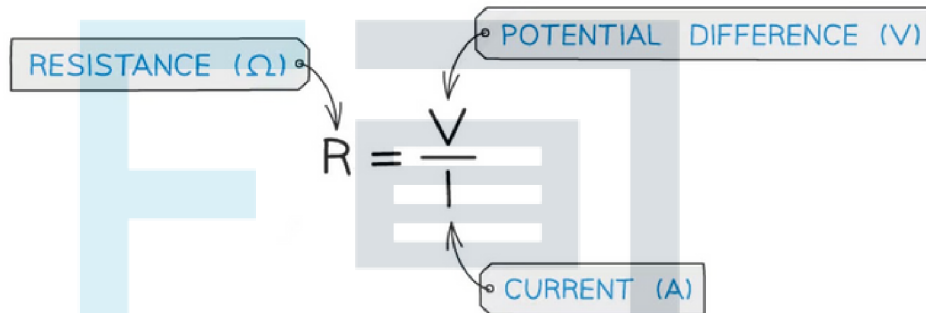
## Resistance

- Resistance is defined as the **opposition** to current
  - For a given potential difference: **The higher the resistance the lower the current**
- Wires are often made from copper because copper has a **low** electrical resistance. This is also known as a **good conductor**
- The resistance  $R$  of a conductor is defined as the ratio of the potential difference  $V$  across to the current  $I$  in it



The diagram shows the formula  $R = \frac{V}{I}$ . Three callout boxes with arrows point to the variables: 'RESISTANCE ( $\Omega$ )' points to  $R$ , 'POTENTIAL DIFFERENCE (V)' points to  $V$ , and 'CURRENT (A)' points to  $I$ .

**Resistance of a component is the ratio of the potential difference and current**

- Resistance is measured in **Ohms ( $\Omega$ )**
- An Ohm is defined as **one volt per ampere**
- The resistance controls the size of the current in a circuit
  - A **higher** resistance means a **smaller** current
  - A **lower** resistance means a **larger** current
- All electrical components, including wires, have some value of resistance



### Exam Tip

Although all electrical components have resistance, the resistance of wires is taken to be **zero** in exam questions.

## 5.1.2 Current–Voltage Characteristics

### Ohm's Law

- Ohm's law states:

**For a conductor at a constant temperature, the current through it is proportional to the potential difference across it**

- Constant temperature implies constant resistance
- Ohm's law is represented in the equation below:


POTENTIAL DIFFERENCE (V)

CURRENT (A)

$V = IR$

RESISTANCE ( $\Omega$ )

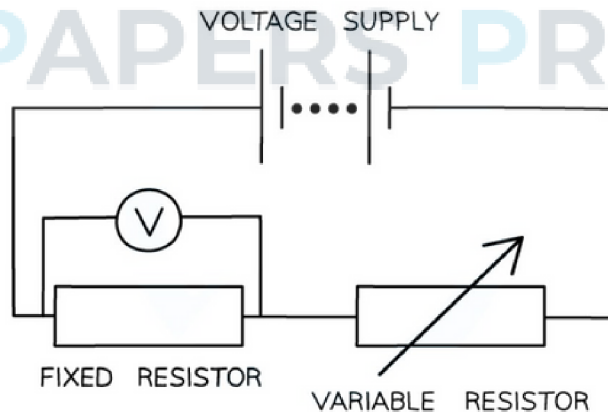
- The relation between potential difference across an electrical component (in this case, a fixed resistor) and the current can be investigated through a circuit such as the one below


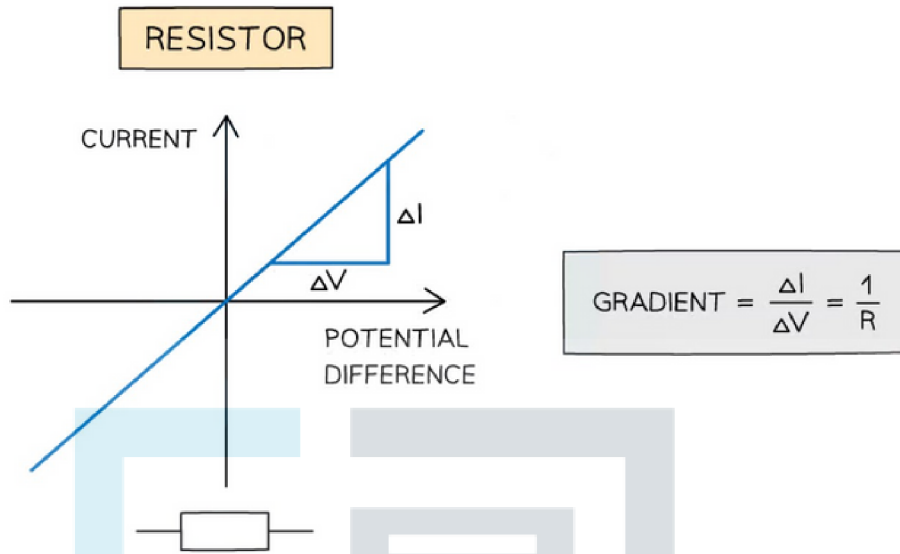
#### ***Circuit for plotting graphs of current against voltage***

- By adjusting the resistance on the variable resistor, the current and potential difference will vary in the circuit
- Measuring the variation of current with potential difference through the fixed resistor will produce a straight line graph, such as the one below






**Circuit for plotting graphs of current against voltage**


- Since the gradient is constant, the resistance  $R$  of the resistor can be calculated by using  $\frac{1}{\text{gradient}}$  of the graph
- An electrical component obeys Ohm's law if its graph of current against potential difference is a **straight line** through the origin
  - A resistor **does** obey Ohm's law
  - A filament lamp does **not** obey Ohm's law
- This applies to any metal wires, provided that the current isn't large enough to increase their temperature
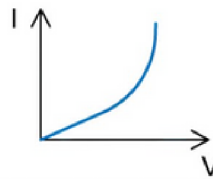
### ? Worked Example

The current flowing through a component varies with the potential difference  $V$  across it as shown.



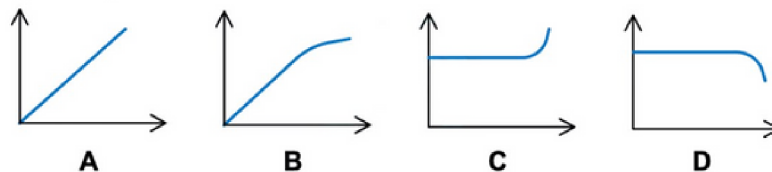Which graph best represents how the resistance  $R$  varies with  $V$ ?



ANSWER: D

STEP 1


USE OHM'S LAW TO FIND R IN TERMS OF V AND I

$$V = IR \text{ THEREFORE } R = \frac{V}{I}$$

STEP 2

THIS MEANS THE GRADIENT OF THE I-V GRAPH IS EQUAL TO  $\frac{1}{R}$

STEP 3

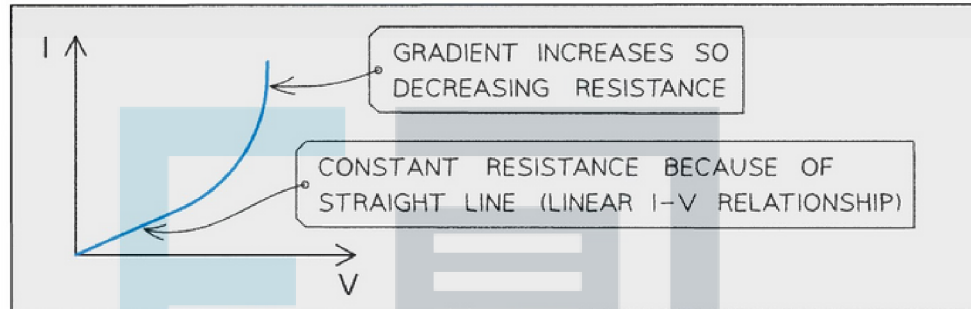

STEP 4


HOW THIS RELATES TO R-V GRAPH

THE INITIAL LINE WILL BE HORIZONTAL SINCE RESISTANCE IS CONSTANT  
 THE LINE WILL THEN CURVE DOWNWARDS AS R DECREASES  
 OPTION D IS THE BEST DESCRIPTION OF THIS



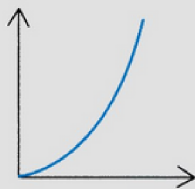
### Exam Tip


- In maths, the gradient is the **slope** of the graph
- The graphs below show a summary of how the slope of the graph represents the gradient




INCREASING GRADIENT

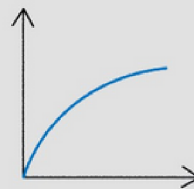

DECREASING GRADIENT

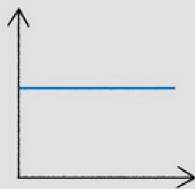


NO GRADIENT

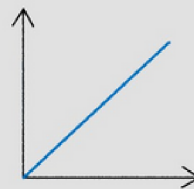

CONSTANT GRADIENT
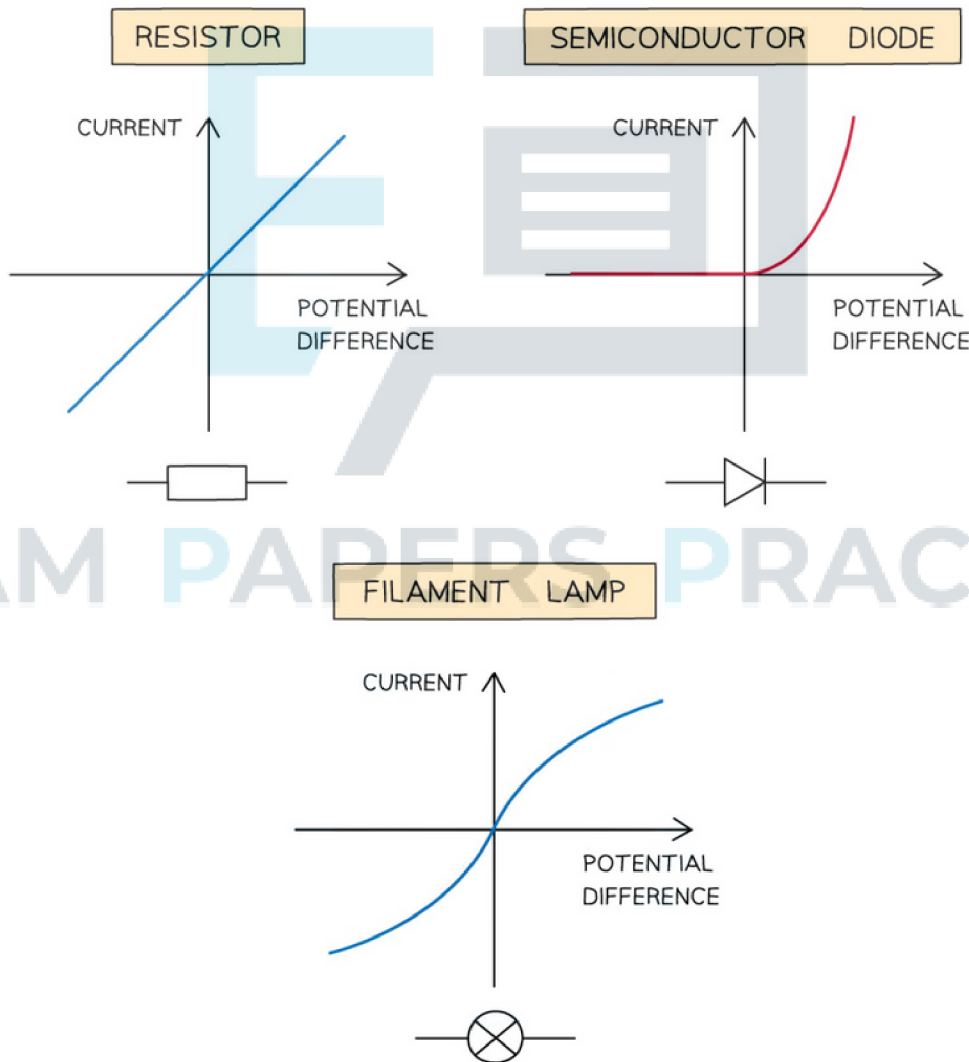
## I-V Characteristics

- As the potential difference (voltage) across a component is increased, the current also increases (by Ohm's law)
- The precise relationship between voltage and current is different for different components and can be shown on an I-V graph
  - For an ohmic conductor, the I-V graph is a straight line through the origin
  - For a semiconductor diode, the I-V graph is a horizontal line that goes sharply upwards
  - For a filament lamp, the I-V graph has an 'S' shaped curve



***I-V characteristics for an ohmic conductor (e.g. resistor), semiconductor diode and filament lamp***

### Ohmic Conductor

- The I-V graph for an ohmic conductor at constant temperature e.g. a resistor is very simple:
  - The current is **directly proportional** to the potential difference
  - This is demonstrated by the **straight-line** graph through the origin

## Semiconductor Diode

- The  $I$ - $V$  graph for a semiconductor diode is slightly different. A diode is used in a circuit to allow current to flow only in a specific direction:
  - When the current is in the direction of the arrowhead symbol, this is **forward bias**. This is shown by the sharp increase in potential difference and current on the right side of the graph
  - When the diode is switched around, it does not conduct and is called **reverse bias**. This is shown by a zero reading of current or potential difference on the left side of the graph


## Filament Lamp

- The  $I$ - $V$  graph for a filament lamp shows the current increasing at a proportionally slower rate than the potential difference
- This is because:
  - As the current increases, the **temperature** of the filament in the lamp **increases**
  - Since the filament is a metal, the higher temperature causes an **increase in resistance**
  - Resistance opposes the current, causing the **current to increase at a slower rate**
- Where the graph is a straight line, the resistance is constant
- The resistance increases as the graph curves
- The filament lamp obeys Ohm's Law for small voltages


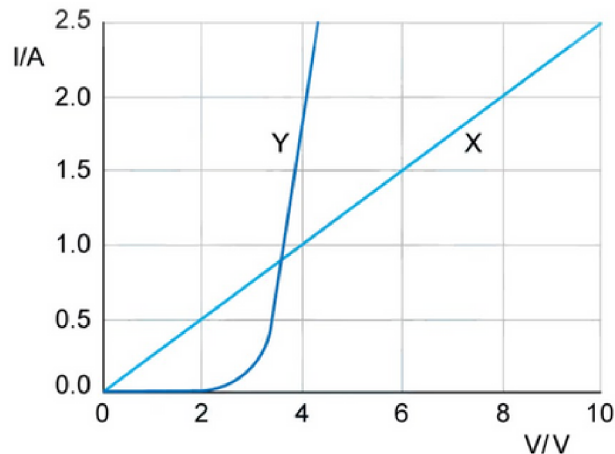
### Worked Example

The  $I$ - $V$  characteristic of two electrical component **X** and **Y** are shown.



Which statement is correct? **A.** The resistance of **X** increases as the current increases

- B.** At 2 V, the resistance of **X** is half the resistance of **Y**
- C.** **Y** is a semiconductor diode and **X** is a resistor
- D.** **X** is a resistor and **Y** is a filament lamp

**ANSWER: C**

- The  $I$ - $V$  graph **X** is **linear**
  - This means the graph has a constant gradient.  $I/V$  and the resistance is therefore also constant (since gradient =  $1/R$ )
  - This is the  $I$ - $V$  graph for a conductor at constant temperature e.g. a resistor
- The  $I$ - $V$  graph **Y** starts with zero gradient and then the gradient increases rapidly
  - This means it has infinite resistance at the start which then decreases rapidly
  - This is characteristic of a device that only has current in one direction e.g. a semiconductor diode
- Therefore, the answer is **C**



#### Exam Tip

Make sure you're confident in drawing the  $I$ - $V$  characteristics for different components, as you may be asked to sketch these from memory in exam questions