

Circuits & The Potential Divider

Mark Scheme

Level	A Level
Subject	Physics
Exam Board	AQA
Paper Type	Multiple Choice

Time Allowed : 30min

1. D
2. B
3. C
4. B
5. A
6. C
7. D
8. D
9. B
10. C
11. D
12. C
13. B
14. A
15. A
16. B
17. D
18. C
19. D
20. D