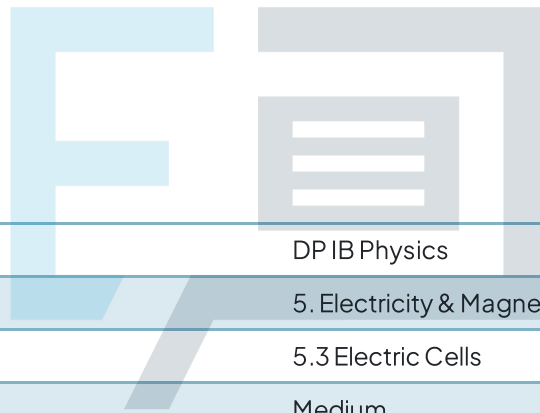




## 5.3 Electric Cells

### Mark Schemes



Course	DP IB Physics
Section	5. Electricity & Magnetism
Topic	5.3 Electric Cells
Difficulty	Medium

# Exam Papers Practice

To be used by all students preparing for DP IB Physics SL  
Students of other boards may also find this useful

1

The correct answer is **C** because:

- A charge of 240 C flows through the resistor in a time of 2 minutes = 120 s
- Calculating current:
  - $I = \frac{\Delta Q}{\Delta t} = \frac{240}{120} = 2 \text{ A}$
- Power dissipated  $P = I^2 R$  and power is defined as the rate of transfer of energy
  - Therefore, energy  $E = P \times t = I^2 R \times t$
  - So,  $1440 = (2)^2 R \times 120$
  - Hence,  $R = \frac{1440}{(2)^2 \times 120} = \frac{12}{480} = 3 \Omega$
- The emf of a circuit  $\epsilon = I(R + r) = 9.0 \text{ V}$ 
  - Therefore, the total resistance in the circuit  $(R + r) = \frac{9.0}{I} = \frac{9.0}{2} = 4.5 \Omega$
- Therefore, since  $R = 3$ 
  - $3 + r = 4.5$
  - Therefore  $r = 4.5 - 3 = 1.5 \Omega$

<b>A</b> is incorrect as	this is the resistance of the resistor and not the internal resistance of the e.m.f.
<b>B</b> is incorrect as	this is the current in the circuit and not the internal resistance of the e.m.f.
<b>D</b> is incorrect as	this is the total resistance in the circuit and not the internal resistance of the e.m.f.

The power dissipated is the energy per time from  $\text{Power} = \frac{\text{Energy}}{\text{Time}}$ . Look carefully that the units 1440 is measured in J, so to calculate the energy use  $\text{Energy} = \text{Power} \times \text{Time}$ .

2

The correct answer is **D** because:

- The electromotive force  $\epsilon$  is defined as the work done per unit charge in moving charge from one terminal of the battery to the other
  - The work, or energy transferred, between terminals is chemical
- The electromotive force can be written as:
  - $\epsilon = \frac{W}{Q}$  such that the energy transferred (or work done)  $W = \epsilon Q$
- However, this chemical energy is deliverable as electrical energy to both the load resistance and the internal resistance
- Therefore,  $\epsilon Q$  is equal to the total energy dissipated in the battery due to the internal resistance as well as externally (the load resistance)

<b>A</b> is incorrect as	the work done around the circuit is not chemical, it is electrical, and is equal to $VQ$ , where $V$ is the terminal potential difference
<b>B</b> is incorrect as	the work done between the terminals is not electric, it is chemical
<b>C</b> is incorrect as	the load resistance is usually given the symbol $R$ . $\epsilon Q$ is a quantity of energy, not resistance

Read each of the answer options carefully and don't just jump to a conclusion without considering them all!

3

The correct answer is **A** because:

- There are two unknowns, so we must set up two unique simultaneous equations
- The emf  $\epsilon = I(R + r) = V + Ir$  where  $V$  is the terminal potential difference
  - Therefore, when  $V = 5.0 \text{ V}$  and  $I = 1.0 \text{ A}$ ,  $\epsilon = 5 + r$  (equation 1)
  - When  $V = 4.0 \text{ V}$  and  $I = 1.5 \text{ A}$ ,  $\epsilon = 4 + 1.5r$  (equation 2)
- Equating the two equations to eliminate  $\epsilon$  gives:
  - $5 + r = 4 + 1.5r$
  - $1 = 0.5r$
  - Therefore,  $r = \frac{1}{0.5} = 2.0 \Omega$
- Using this value for  $r$  in equation 1 gives:
  - $\epsilon = 5 + 2 = 7.0 \text{ V}$

<p><b>B</b> is incorrect as</p>	<p>The internal resistance <math>r = 2 \Omega</math> because <math>1 = 0.5r</math> so, <math>\frac{1}{0.5} = 2.0 \Omega</math> and not <math>0.5 \Omega</math></p>
<p><b>C</b> is incorrect as</p>	<p><math>\epsilon = 5 + 2 = 7.0 \text{ V}</math> and not <math>\epsilon = 5 - 2 = 3.0 \text{ V}</math></p>
<p><b>D</b> is incorrect as</p>	<p>The internal resistance <math>r = 2 \Omega</math> because <math>1 = 0.5r</math> so, <math>\frac{1}{0.5} = 2.0 \Omega</math> and not <math>0.5 \Omega</math></p> <p><math>\epsilon = 5 + 2 = 7.0 \text{ V}</math> and not <math>\epsilon = 5 - 2 = 3.0 \text{ V}</math></p>

If there are **two** unknowns in each question, don't panic! This is a huge flag that you are required to set up **two** simultaneous equations and solve them. In more extended questions, you may even sometimes have **three** unknowns – but as you might expect, this just means you then need to set up **three** unique simultaneous equations and perform a bit more algebra to manipulate and solve them. Anytime you have the same number of unknowns as you have equations – think simultaneous equations!

4

The incorrect statement is **B** because:

- The lifetime of a cell depends on the current drawn from it, not on the amount of charge it stores (a measure of the cell's capacity)
- A cell's capacity can be measured by drawing a constant current until it is discharged
  - The charge delivered during the time it takes to fully discharge is the cells capacity

<b>A</b> is correct as	capacity can be measured by drawing a constant current from a cell until it is discharged. The area under the corresponding current-time graph, which would be the total charge delivered, is a measure of the cell's capacity. A larger current would reduce the lifetime of the cell, not its capacity
<b>C</b> is correct as	larger currents discharge cells more quickly, because cells can only deliver a finite amount of charge to a circuit over its lifetime (its capacity)
<b>D</b> is correct as	the internal resistance of a cell gradually increases over a cell's lifetime, due to several factors, including chemical and structural degradation of the terminals

5

The correct answer is **A** because:

- The cell emf  $\epsilon = I(R + r)$ 
  - Therefore, this can be rearranged into the form of a straight line
  - $I = \frac{\epsilon}{R+r}$  hence  $\frac{1}{I} = \frac{R+r}{\epsilon} = \frac{R}{\epsilon} + \frac{r}{\epsilon}$
  - If  $y = mx + c$ , then  $\frac{1}{I}$  on the  $y$ -axis and  $R$  on the  $x$ -axis is a straight line with a gradient equal to  $\frac{1}{\epsilon}$

<b>B</b> is incorrect as	$I = \frac{\epsilon}{R+r}$ so $\frac{1}{I} = \frac{R+r}{\epsilon} = \frac{R}{\epsilon} + \frac{r}{\epsilon}$ and not $\frac{1}{R} \cdot R$ is a quantity on the $x$ -axis, so it is not possible to have a straight-line graph with a gradient of $\frac{1}{\text{quantity}}$
<b>C</b> is incorrect as	$I = \frac{\epsilon}{R+r}$ so $\frac{1}{I} = \frac{R+r}{\epsilon} = \frac{R}{\epsilon} + \frac{r}{\epsilon}$ and not $\frac{1}{r}$
<b>D</b> is incorrect as	$I = \frac{\epsilon}{R+r}$ so $\frac{1}{I} = \frac{R+r}{\epsilon} = \frac{R}{\epsilon} + \frac{r}{\epsilon}$ and not $r$

You should be comfortable, for the Standard Level Diploma Programme, with recognising linear equations and rearranging them so that they match a given graph. The method for this question is sketched out in more detail below:

$$E = I(R + r)$$

$$I = \frac{E}{R + r}$$

$$\frac{1}{I} = \frac{R + r}{E} = \frac{R}{E} + \frac{r}{E}$$

$$\frac{1}{I} = \frac{1}{E}R + \frac{r}{E}$$

$y = mx + c$

gradient  $\rightarrow$   $\frac{1}{E}$   $\rightarrow$   $\frac{r}{E}$   $\rightarrow$  y-intercept

6

The correct answer is **D** because:

- Applying Kirchhoff's loop law, starting at the negative terminal of the primary cell and moving round the circuit anticlockwise:
  - $\Sigma V = 0 = 10 - 4I - 2 - 4I$
  - Therefore,  $0 = 8 - 8I$
  - $8I = 8$  so  $I = 1\text{A}$
- This means statement C is incorrect
- The power of an emf,  $\epsilon$  is given by  $P = \epsilon I$ 
  - Therefore, the power generated by the primary battery  $P = 10 \times 1 = 10\text{W}$
  - The power stored in the secondary battery  $P = 2 \times 1 = 2\text{W}$
- This means statement B is incorrect, and:
  - Since  $\frac{2}{10} = 0.2 = 20\%$ , statement D is correct



<b>A</b> is incorrect as	primary cells are not rechargeable, only secondary cells are charged from the primary cell
<b>B</b> is incorrect as	this is not true. The power generated in the primary cell is not equal to the power stored in the secondary cell
<b>C</b> is incorrect as	the current in the circuit is 1 A as shown

You should remember that primary cells can only be used once (until it runs out). Therefore, statement A is incorrect. Secondary batteries are rechargeable and can be reused.

7

The incorrect statement is **C** because:

- An ideal battery is one for which the internal resistance is zero
- Hence, since  $\epsilon = I(R + r) = V + Ir$ , where  $V$  is the terminal potential difference,  $I$  is the current and  $r$  is the internal resistance,
  - If the internal resistance is zero, then the terminal potential difference (i.e., that which is measurable) would be exactly equal to the emf  $\epsilon$

<b>A</b> is correct as	non-ideal batteries have internal resistance. Hence, the terminal pd $V = \epsilon - Ir$ , and so is always less than the emf $\epsilon$
<b>B</b> is correct as	$V = \epsilon - Ir$ . Hence, if the current $I = 0$ , then $V = \epsilon$
<b>D</b> is correct as	the terminal potential difference for non-ideal batteries decreases with time as current is drawn from it, due to the battery's internal resistance



8

The incorrect answer is **C** because:

- The internal resistance of a cell must have units equivalent to the ohm,  $\Omega$ 
  - $[R] = \Omega = \frac{[V]}{[I]} = \text{V A}^{-1}$
  - Therefore, option A is correct
- The Volt, V is defined by the equation  $V = \frac{W}{q}$ :
  - $[V] = V = \frac{[W]}{[q]} = \text{J C}^{-1}$
  - Since  $[Q] = [I][t]$ , then  $C = \text{As}$
  - Substituting this into  $\Omega = \text{V A}^{-1} = (\text{J C}^{-1}) \text{A}^{-1} = \text{J} (\text{A}^{-1} \text{s}^{-1}) \text{A}^{-1}$
  - Therefore,  $\Omega = \text{J s}^{-1} \text{A}^{-2}$  so option B is correct
- The Joule, J is defined by the equation  $W = Fd$ :
  - $[W] = [F][d] = \text{N m}$
  - Since  $[F] = [m][a]$  then  $[F] = \text{N} = \text{kg m s}^{-2}$
  - Substituting this into  $[W] = \text{J} = \text{N m} = (\text{kg m s}^{-2}) \text{m} = \text{kg m}^2 \text{s}^{-2}$
  - Therefore,  $\Omega = (\text{kg m}^2 \text{s}^{-2}) \text{s}^{-1} \text{A}^{-2} = \text{kg m}^2 \text{A}^{-2} \text{s}^{-3}$
- Therefore, option D is correct
  - So, option C cannot be units for internal resistance

Make sure you read this question carefully. It says incorrect and not correct. Do not just start and then assume A is correct.

9

The correct answer is **B** because:

- The terminal potential difference  $V_X$  and  $V_Y$  can be written in terms of the emf  $\epsilon$ :
  - Treating the circuit as a potential divider, with the  $3\ \Omega$  resistor in series with the internal resistance  $r = 0.5\ \Omega$ , then  $V_X = \epsilon \times \frac{R}{R+r} = \frac{1.5 \times 3}{3+0.5} = \frac{9}{7}$
  - Similarly,  $V_Y = \epsilon \times \frac{R}{R+r} = \frac{3 \times 1.5}{3+2} = \frac{9}{10}$
  - Therefore,  $V_X > V_Y$  since the denominator is smaller for  $V_X$
- The power dissipated across the resistor,  $P_X$  and  $P_Y$ , can be written in terms of the terminal potential differences  $V_X$  and  $V_Y$ :
  - $P_X = \frac{V_X^2}{R} = \frac{V_X^2}{3}$
  - $P_Y = \frac{V_Y^2}{R} = \frac{V_Y^2}{3}$
  - Since  $V_X > V_Y$ ,  $P_X > P_Y$
  - Therefore, row B is correct

<b>A</b> is incorrect as	the power is greater in X than in Y. Consider the equation for power, $P = IV$ then if $V$ is greater then $P$ will also be greater.
<b>C</b> is incorrect as	both the power and potential difference are greater in X than in Y, as $V_X > V_Y$ as $\frac{9}{7} > \frac{9}{10}$  and consider the equation for power, $P = IV$ then if $V$ is greater then $P$ will also be greater.

<b>D</b> is correct as	the potential difference is greater in X than in Y, as $V_X > V_Y$ as $\frac{9}{7} > \frac{9}{10}$
------------------------	--

10

The correct answer is **D** because:

- The terminal potential difference  $V = \epsilon - Ir$ 
  - If the resistance  $R$  decreases, then current in the circuit increases
  - Therefore, the terminal potential difference  $V$  decreases as well
  - The power dissipated in the cell (that is, across the internal resistance)
 
$$P = I^2 r$$
, which therefore becomes large
- Hence, statement (1) is correct
- If the resistance  $R$  is made very large, this causes a very small current in the circuit
  - The power supplied by the cell  $P = \epsilon I = I^2(R + r) = I^2 R + I^2 r$
  - The power dissipated by the resistor  $R$  is given by the term  $I^2 R$ , which dominates since  $R$  is now very large
  - Therefore, most of the power supplied by the cell is dissipated across the resistor  $R$
- Hence, statement (2) is correct
- If the resistance of  $R$  is made very small, then the current in the circuit will increase
  - Hence, the charge delivered by the cell (its capacity) will rapidly deplete, resulting in a shorter lifetime

Walking through each step in this question is useful practise for you to understand the difference components of a circuit, in terms of the external (or load) resistance  $R$  and the internal resistance  $r$ . Imagining these as two distinct components, over which power supplied by the emf of the cell is dissipated, is very good exam technique.