
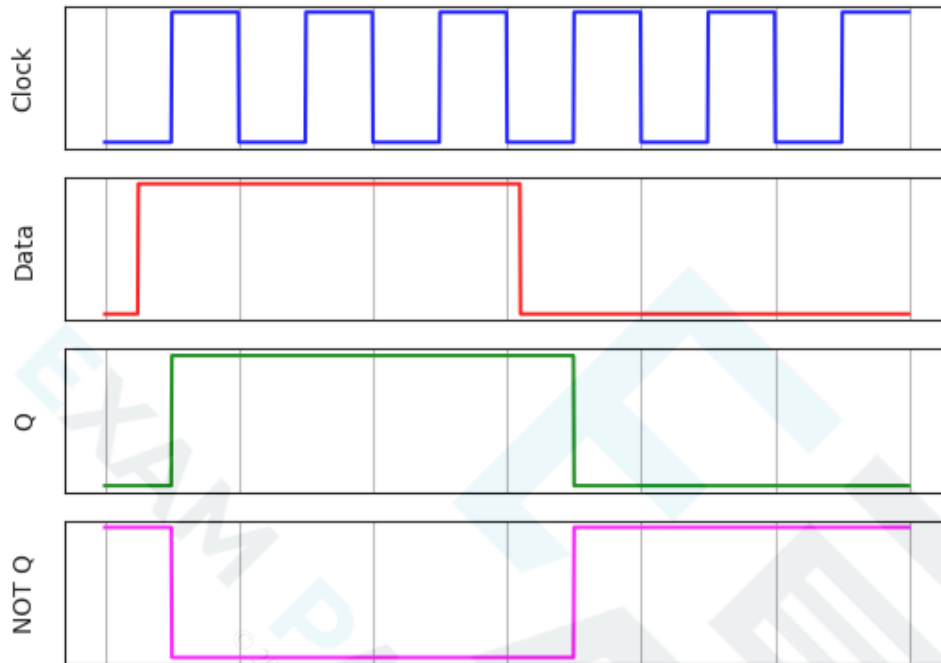


D Type Flip Flop Worksheet

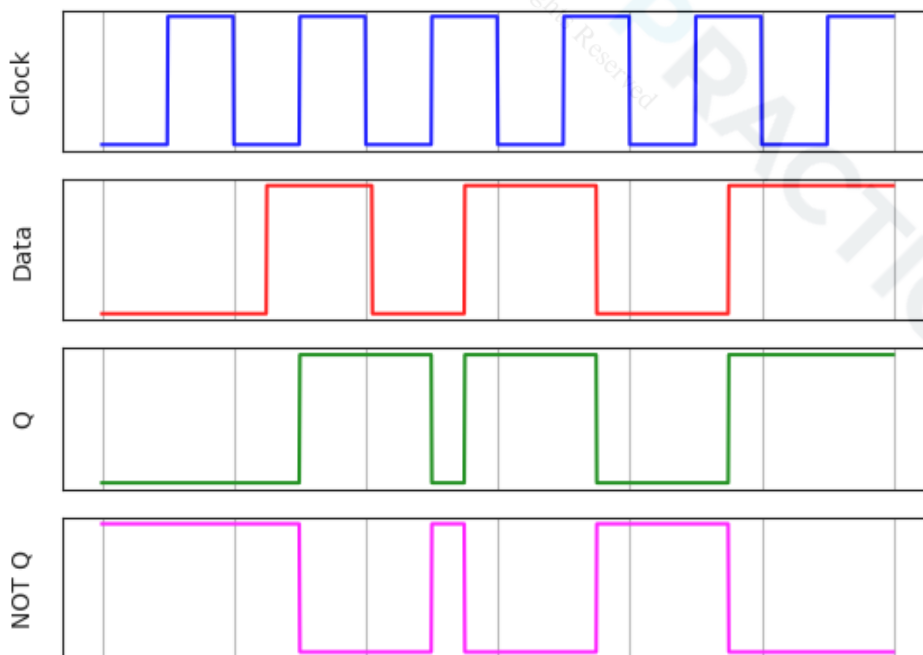1) Draw the output plot for the level triggered D type flip flop




2a) Draw the output plot for the level triggered D type flip flop




2b) Draw the output plot for the edge triggered D type flip flop

D Type Flip Flop Worksheet

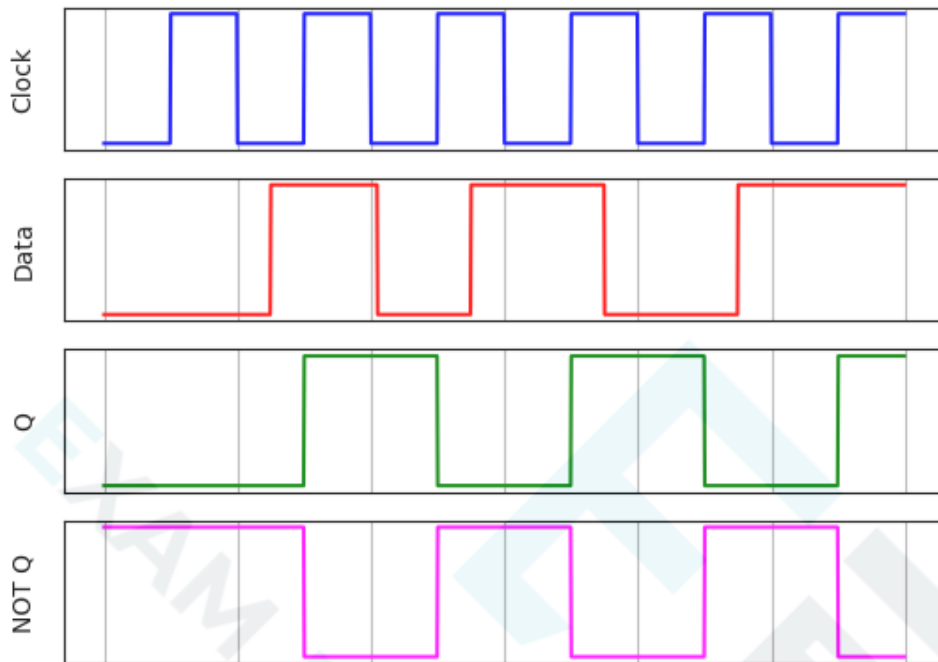


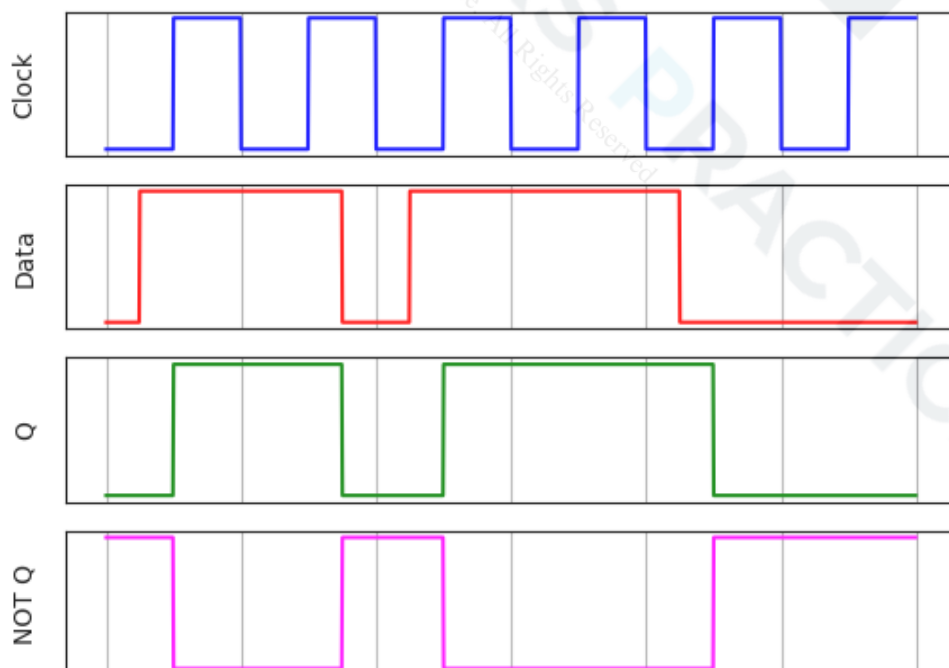3a) Draw the output plot for the level triggered D type flip flop



3b) Draw the output plot for the edge triggered D type flip flop

D Type Flip Flop Worksheet

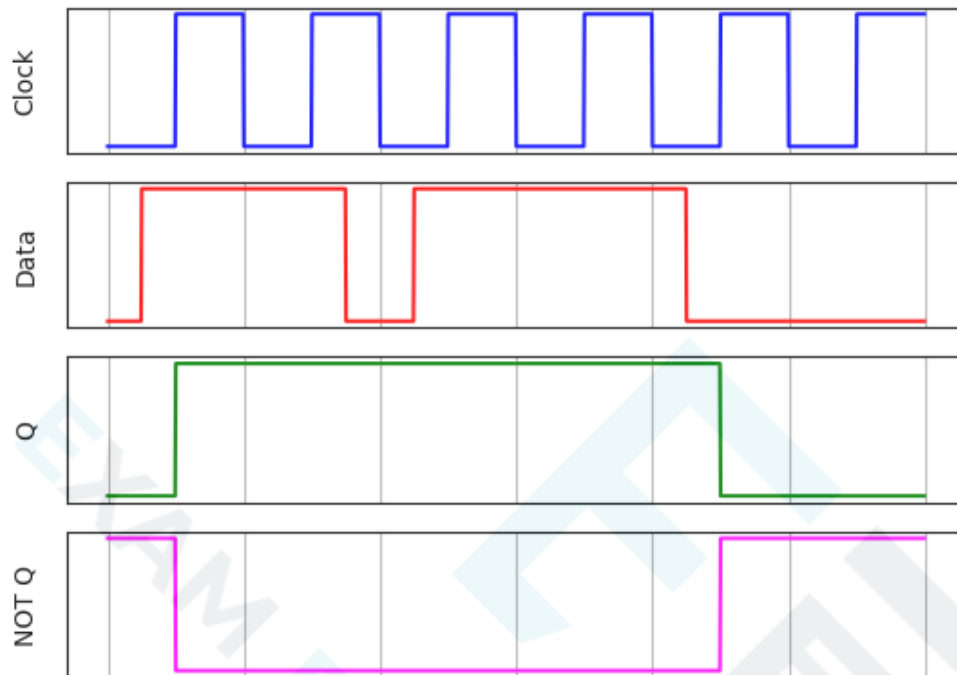

© 2025 Exam Papers Practice. All Rights Reserved