



6.4 Logic gates

Name: _____

Class: _____

Date: _____


Time: **118 minutes**

Marks: **115 marks**

Comments:

Q1.

The diagram shows a logic circuit.

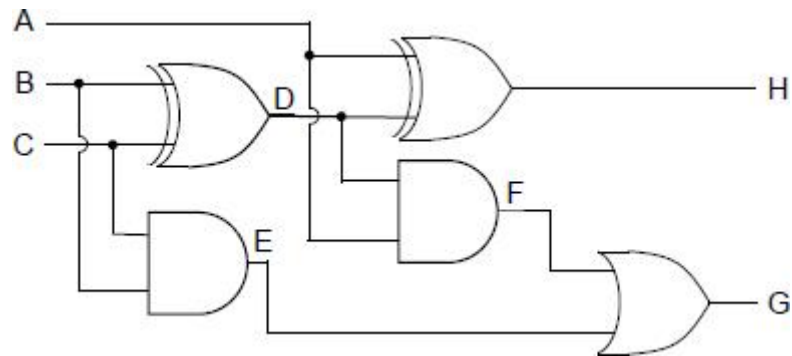

- (a) Complete the part of the truth table for the circuit in the diagram that is shown below.

Inputs							Outputs	
A	B	C	D	E	F	G	H	
0	0	0						
0	0	1						
0	1	1						
1	1	1						

(3)

- (b) Using the diagram above, write a Boolean expression to show how the output **G** is calculated from the inputs **A**, **B** and **C**.

EXAM PAPERS PRACTICE

G = _____

(3)

- (c) Explain the purpose of the circuit.

(1)

(Total 7 marks)

Q2.

A burglar alarm system is to be implemented that has the following sensors:

- a door sensor **D** that outputs TRUE when the door is open and FALSE when the door is shut

- a pressure mat sensor **M** that outputs TRUE while a weight is detected on it and FALSE when no weight is detected on it.

The alarm also has a key **K** that turns the alarm on and off. **K** outputs a TRUE signal when the alarm is switched on and FALSE when the alarm is off.

The alarm output **A** sounds a bell. It should be TRUE if:

- the alarm is on AND
- either of the sensors **D** or **M** are set to the value TRUE.

- (a) Draw a logic circuit that will behave as described above for the inputs **D**, **M** and **K** and the output **A**.



(2)

- (b) Write a Boolean expression to represent the logic of this alarm system.

A= _____

(2)

- (c) In this alarm system, the alarm bell will sound only while the door is open or a weight is placed on the pressure mat. If someone who has stepped on to the mat moves off it, or an open door is closed, the alarm bell will stop ringing.

A D-type flip-flop could be incorporated into the logic circuit so that the alarm bell would continue to sound after a person closed the door or moved off the pressure mat.

Explain how this could be achieved. In your answer refer to:

- why a D-type flip-flop would be suitable for this task
- where the D-type flip-flop would need to be inserted into the circuit
- what additional input the D-type flip-flop would need.

(3)
(Total 7 marks)

Q3.

- (a) Complete the truth table below for a NAND gate.

NAND gate		
Input A	Input B	Output
0	0	
0	1	
1	0	
1	1	

(1)

- (b) Multiplexors are used in electronic switching.

A 2-to-1 multiplexor has a Boolean equation where A and B are two inputs, S is the selector input, and Q is the output.

$$Q = (A \cdot \bar{S}) + (B \cdot S)$$

- (i) Complete the truth table for the above Boolean equation.

S	A	B	\bar{S}	$A \cdot \bar{S}$	$B \cdot S$	Q
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

(3)

- (ii) Draw a circuit for the Boolean equation in the rectangle below.



(4)

- (iii) By considering its inputs and outputs, describe what the 2-to-1 multiplexor circuit does.

(1)

(Total 9 marks)

Q4.

- (a) Complete the truth tables for the following logic gates.

OR gate

Input A	Input B	Output
0	0	
0	1	
1	0	
1	1	

NAND gate


Input A	Input B	Output
0	0	
0	1	

1	0	
1	1	

(2)

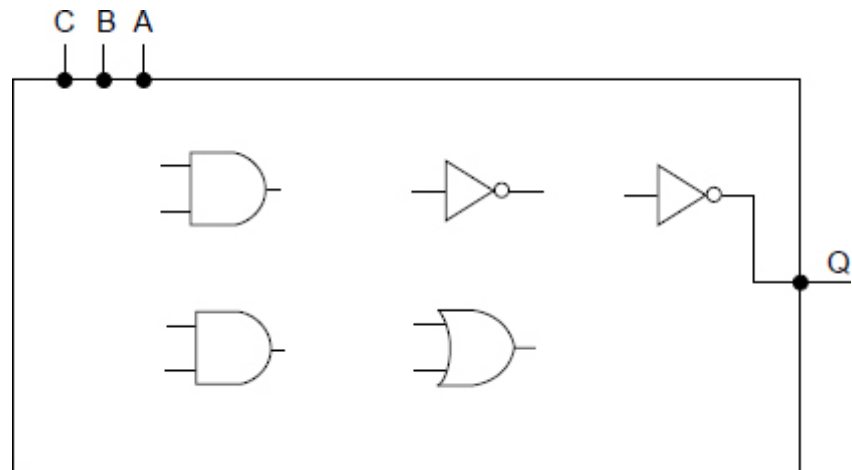- (b) Represent the following Boolean equation as a logic circuit by completing the diagram below.

$$Q = \overline{\overline{A \cdot B} + B \cdot C}$$



(5)

- (c) Simplify the following expression.

$$\overline{\overline{A} + \overline{B}} + B \cdot \overline{A}$$

Show each stage of your working.

(2)

EXAM PAPERS PRACTICE

Final answer _____

(1)

(Total 10 marks)

Q5.

- (a) State the names of the logic gates represented by each of the three truth tables below.

Input A	Input B	Output
0	0	0
0	1	0

Logic gate name _____

1	0	0
1	1	1

Input A	Input B	Output
0	0	1
0	1	0
1	0	0
1	1	0

Logic gate name _____

Input A	Input B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Logic gate name _____

(3)

(b) Simplify the following Boolean expressions.

(i) $B \cdot (A + \bar{A})$

EXAM PAPERS PRACTICE

(1)

(ii) $A \cdot B + B$

(1)



(iii) $\bar{B} \cdot (\bar{A} + \bar{B})$

(2)

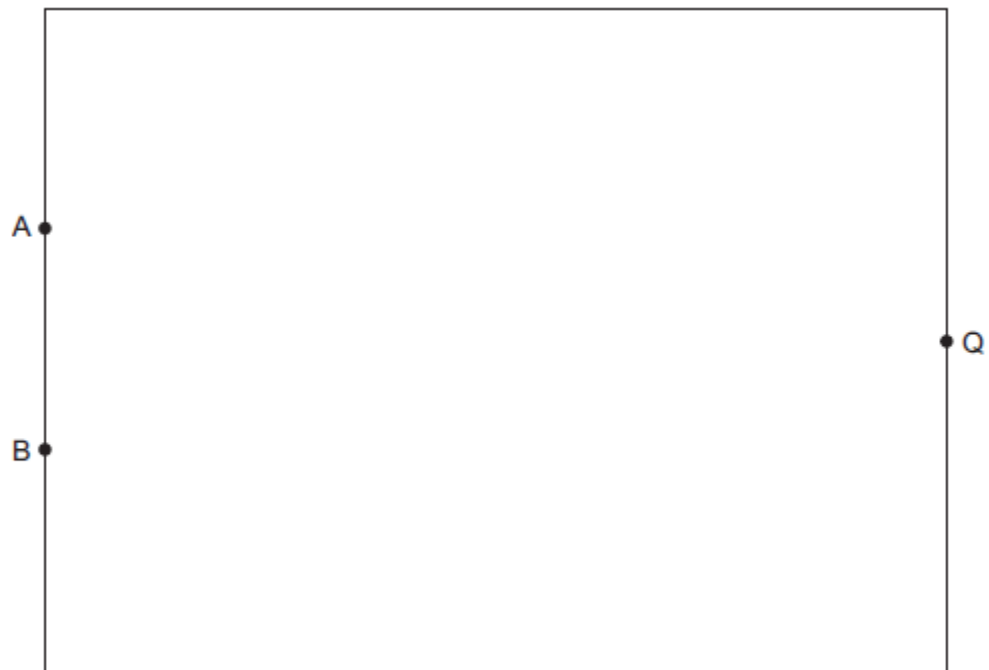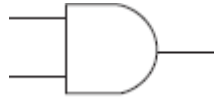(c) Draw a logic circuit for the following Boolean expression:

$$Q = (A \oplus B) \cdot B$$



You will need to make use of the symbols below when drawing your logic circuit.



(2)
(Total 9 marks)

Q6.

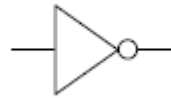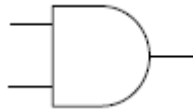- (a) Represent the Boolean equation $Q = \overline{A} \cdot \overline{B}$ as a logic circuit by drawing a diagram using **only** the following symbols:



AND

NOT



(3)

- (b) Use the following truth tables to demonstrate that $A + B = \overline{\overline{A} \cdot \overline{B}}$

A	B	A + B	A	B				$\overline{\overline{A} \cdot \overline{B}}$
0	0		0	0				
0	1		0	1				
1	0		1	0				
1	1		1	1				

(4)

- (c) What is the name commonly associated with the statement $A + B = \overline{\overline{A} \cdot \overline{B}}$?

EXAM PAPERS PRACTICE

(1)

- (d) Simplify the Boolean expression below.

$$A.B.\overline{C} + A.\overline{C}$$

Show each stage of your workin.

(2)

Final answer _____

(1)

(Total 11 marks)

Q7.

- (a) Complete the truth tables for the following logic gates.

AND Gate		
Input X	Input Y	Input Q
0	0	
0	1	
1	0	
1	1	

XOR Gate		
Output X	Input Y	Output Q
0	0	
0	1	
1	0	
1	1	

(2)

- (b) A line-following robot has three sensors. It moves along a black line on a white background whilst the following conditions are met:

- the ultrasonic sensor U does not detect any obstacle
- either, but not both, of the infrared sensors L and R are on the black line.

Sensor U returns 1 if it detects an obstacle and 0 if the path is clear.

Sensors L and R each return 1 if they detect black and 0 if they detect white.

A logic circuit will process the input from the sensors and produce an output M.


M should be 1 if the robot is to move and 0 if the robot should stop.

- (i) Represent the output M as a Boolean expression.

M = _____

(3)

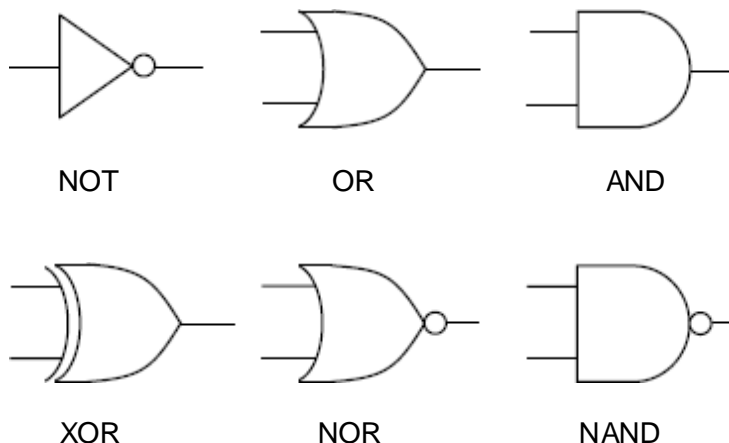- (ii) The following symbols are used to represent logic gates:



Using a combination of any of the above logic gates draw a logic circuit for this system in the box below. You will **not** need to use all of the different types of logic gates.



(3)

- (c) Apply De Morgan's Law(s) to the following expression and simplify the result.

$$Q = \overline{\overline{A} + (B \cdot A)}$$

Show the stages of your working.

(2)

Final answer


EXAM PAPERS PRACTICE

(1)

(Total 11 marks)

Q8.

The diagram below shows a logic circuit.

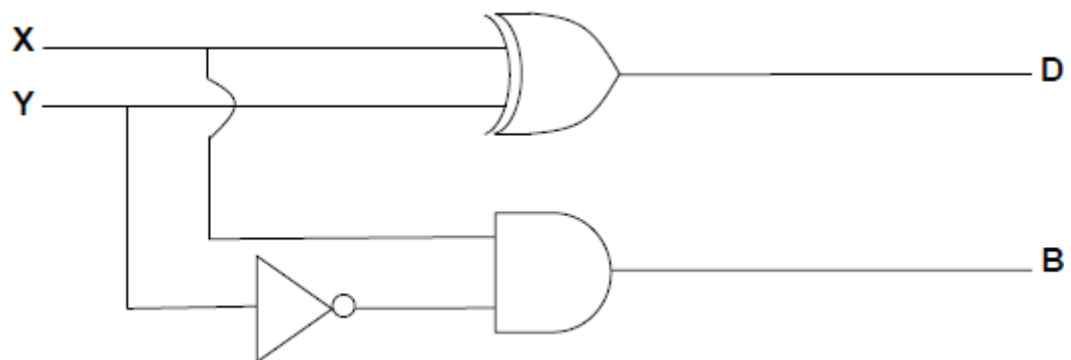


- (a) Write a Boolean expression for **D**.

(1)

- (b) Write a Boolean expression for **B**.

(1)

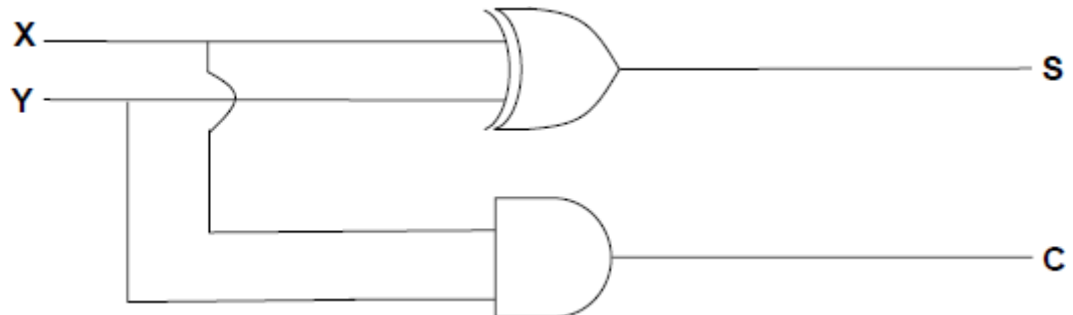- (c) The diagram below shows a different logic circuit.



- (i) Complete the truth table below for the logic circuit in the diagram above.

Inputs		Outputs	
X	Y	C	S
0	0		
0	1		
1	0		
1	1		

(2)

- (ii) What arithmetic function does the logic circuit in the diagram above perform?

(1)

- (d) **Without** using a truth table, simplify the Boolean expression below.

$$(X + Y) \cdot (X + \bar{Y})$$

Show the stages of your working.

(3)

Final answer _____

(1)

(Total 9 marks)

Q9.


- (a) Complete the truth tables for the following logic gates.

NAND Gate		
Input X	Input Y	Output Q
0	0	
0	1	
1	0	
1	1	

NOR Gate		
Input X	Input Y	Output Q
0	0	
0	1	
1	0	
1	1	

(2)

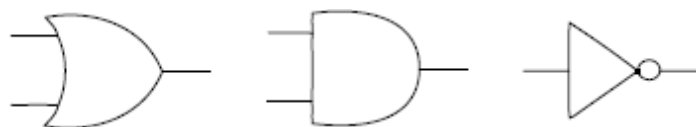- (b) Represent the Boolean equation $Z = \bar{A} \cdot \bar{B} + C$ in the form of a logic circuit by drawing a diagram using the following symbols.



OR

AND

NOT



(3)

- (c) Simplify the Boolean expression below.

$$\overline{(A \cdot B)} + (\overline{A} \cdot \overline{B})$$

Show each stage of your working.

EXAM PAPERS PRACTICE

(3)


Final answer _____

(1)

(Total 9 marks)

Q10.

The diagram below shows a logic circuit.

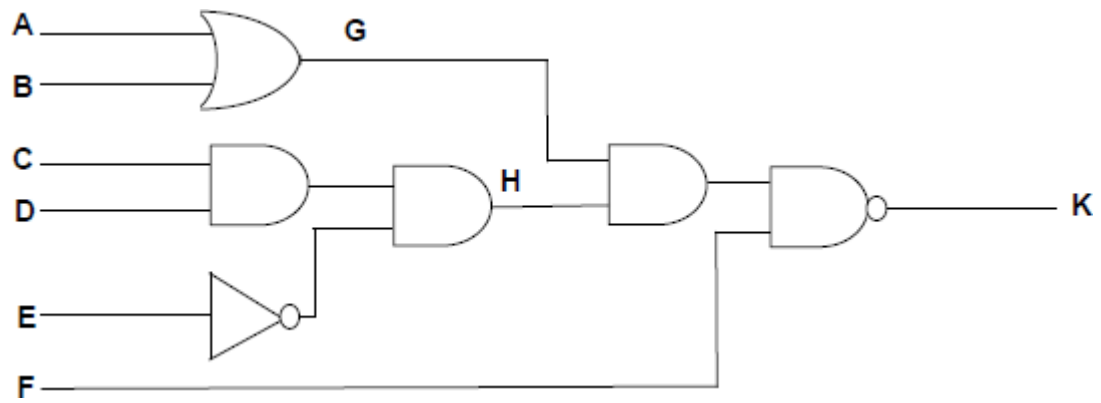

Complete the truth table for the inputs that have been given.

Inputs								
A	B	C	D	E	F	G	H	K
0	0	1	1	0	0			
0	1	1	1	0	1			
1	0	1	1	1	0			
1	1	1	1	1	1			

(Total 3 marks)

Q11.

(a) Complete the truth tables for the following logic gates.

OR Gate		
Input A	Input B	Output Q
0	0	
0	1	
1	0	
1	1	

XOR Gate		
Input A	Input B	Output Q
0	0	
0	1	
1	0	
1	1	

(2)

(b) Represent the Boolean equation $Q = A + B \cdot \bar{C}$ as a logic circuit by drawing a diagram of it.



(3)

- (c) Simplify the Boolean expression:

$$B \cdot (A + \overline{B})$$

Show your working.


(3)

(Total 8 marks)

EXAM PAPERS PRACTICE

Q12.

The figure below shows a logic circuit.

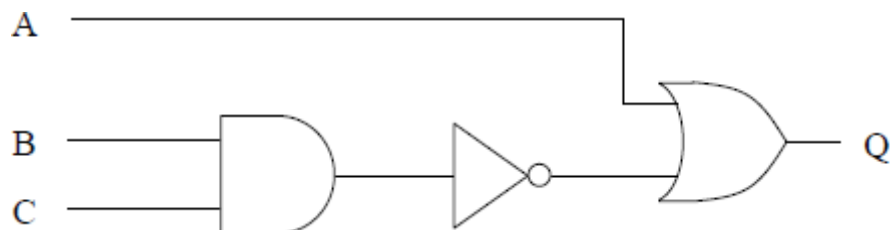

- (a) Complete the truth table below for the logic circuit shown in the above figure. Write the correct value of the output Q for each of the listed sets of inputs.

Input A	Input B	Input C	Output Q
1	0	1	

0	1	0	
0	1	1	

(3)

- (b) Two of the gates in the circuit shown in the above figure could be replaced by a single gate.

- (i) Which **two** gates could be replaced?

(1)

- (ii) What single gate would be used instead?

(1)

- (c) Why is it an advantage to use as few gates as possible in a logic circuit?

(1)

(Total 6 marks)

Q13.

- (a) Look at the truth table below.

Input A	Input B	Output Q
0	0	1
0	1	0
1	0	0
1	1	0

What logic gate does the table represent?

(1)

- (b) An interior light in a two-door car is controlled by two switches that the driver can turn on or off and two sensors, one per door.

The switches are named A and B.

The door sensors are named C and D.


The interior light is named L.

If a door is open the output of its sensor is on.


If a door is closed the output of its sensor is off.

- If both switches A and B are off then the light L is always off.
- If switch A is on the light L is always on.
- If switch B is on and switch A is off then:
 - the light L turns on if one or more of the car doors is opened
 - the light L turns off if both of the doors are closed.

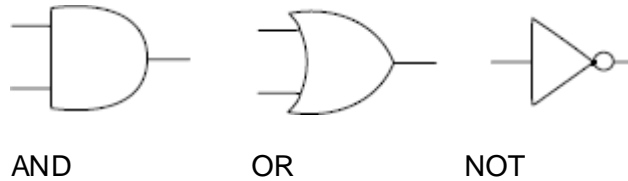The following symbols are used to represent logic gates:



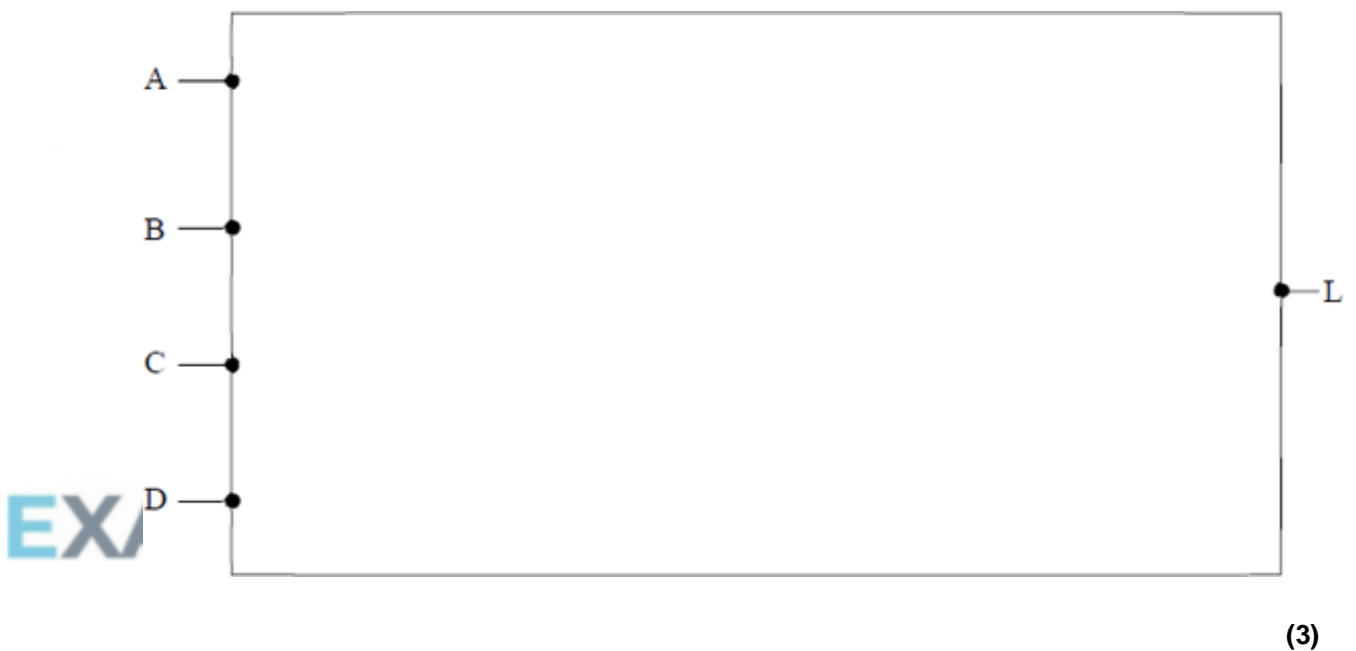- (i) Using only AND, OR and NOT gates draw a logic circuit for this system in the box below. You may not need to use all three types of gate.



- (ii) Write a Boolean expression to represent the logic of the interior light system.

_____ (1)

- (c) Simplify the Boolean expression below, showing your working.

$$\overline{\overline{A} + \overline{B}} + B \cdot \overline{A}$$

(3)
(Total 8 marks)

Q14.

- (a) Complete the truth tables for the following logic gates.

OR gate

Input A	Input B	Output
0	0	
0	1	
1	0	
1	1	

AND gate

Input A	Input B	Output
0	0	
0	1	
1	0	
1	1	

(2)

- (b) (i) A single output Q is produced from three inputs A, B and C. Output Q is required to be 1 only if inputs A and B are 1, or input C is 1 and input B is 0.


Express this as a Boolean equation.

EXAM PAPERS PRACTICE

Q = _____

(2)

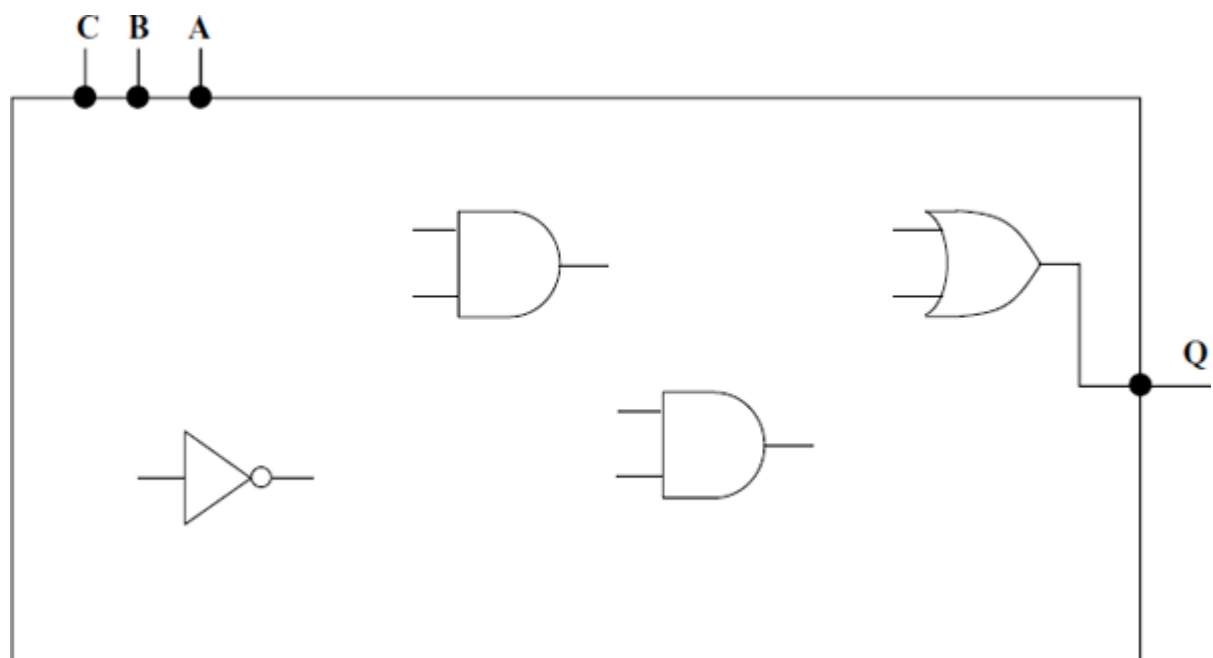- (ii) Represent this Boolean equation diagrammatically by completing the logic gate diagram below.



(4)
(Total 8 marks)

