



## 6.5 Boolean algebra

Name: \_\_\_\_\_

Class: \_\_\_\_\_

Date: \_\_\_\_\_

---

Time: **126 minutes**


Marks: **121 marks**

Comments:

---

**Q1.**

The diagram shows a logic circuit.

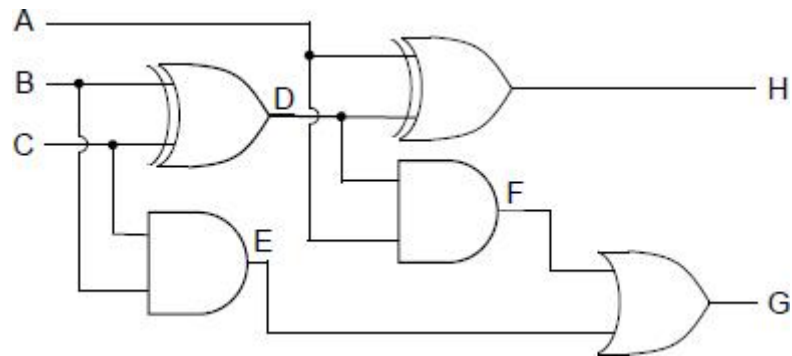

- (a) Complete the part of the truth table for the circuit in the diagram that is shown below.

Inputs								Outputs	
A	B	C	D	E	F	G	H		
0	0	0							
0	0	1							
0	1	1							
1	1	1							

(3)

- (b) Using the diagram above, write a Boolean expression to show how the output **G** is calculated from the inputs **A**, **B** and **C**.

**EXAM PAPERS PRACTICE**

G = \_\_\_\_\_

(3)

- (c) Explain the purpose of the circuit.

\_\_\_\_\_  
 \_\_\_\_\_

(1)

(Total 7 marks)

**Q2.**

- (a) Complete the table below and draw the symbol for an AND gate in the box.

AND gate symbol

Input A	Input B	Output

AND gate symbol

(b) Using the laws of Boolean algebra, simplify the following Boolean expression.

A.B. (A + B)

### Answer

(c) Using the laws of Boolean algebra, simplify the following Boolean expression.

$$(X + Y).(X + \overline{Y})$$

Answer \_\_\_\_\_

**(Total 8 marks)**

**Q3.**

A burglar alarm system is to be implemented that has the following sensors:

- a door sensor **D** that outputs TRUE when the door is open and FALSE when the door is shut
- a pressure mat sensor **M** that outputs TRUE while a weight is detected on it and FALSE when no weight is detected on it.

The alarm also has a key **K** that turns the alarm on and off. **K** outputs a TRUE signal when the alarm is switched on and FALSE when the alarm is off.

The alarm output **A** sounds a bell. It should be TRUE if:

- the alarm is on AND
- either of the sensors **D** or **M** are set to the value TRUE.

- (a) Draw a logic circuit that will behave as described above for the inputs **D**, **M** and **K** and the output **A**.



(2)

- (b) Write a Boolean expression to represent the logic of this alarm system.

**A**= \_\_\_\_\_

(2)

- (c) In this alarm system, the alarm bell will sound only while the door is open or a weight is placed on the pressure mat. If someone who has stepped on to the mat moves off it, or an open door is closed, the alarm bell will stop ringing.

A D-type flip-flop could be incorporated into the logic circuit so that the alarm bell would continue to sound after a person closed the door or moved off the pressure mat.

Explain how this could be achieved. In your answer refer to:

- why a D-type flip-flop would be suitable for this task
- where the D-type flip-flop would need to be inserted into the circuit
- what additional input the D-type flip-flop would need.

---



---



---



---



---

(3)  
(Total 7 marks)

**Q4.**

- (a) Complete the truth table below for a NAND gate.

NAND gate		
Input A	Input B	Output
0	0	
0	1	
1	0	
1	1	

(1)

- (b) Multiplexors are used in electronic switching.

A 2-to-1 multiplexor has a Boolean equation where A and B are two inputs, S is the selector input, and Q is the output.

$$Q = (A.\bar{S}) + (B.S)$$

- (i) Complete the truth table for the above Boolean equation.

S	A	B	$\bar{S}$	$A.\bar{S}$	$B.S$	Q
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				

(3)

- (ii) Draw a circuit for the Boolean equation in the rectangle below.



(4)

- (iii) By considering its inputs and outputs, describe what the 2-to-1 multiplexor circuit does.

---



---



---

(1)

(Total 9 marks)

**Q5.**

- (a) Complete the truth tables for the following logic gates.

OR gate

Input A	Input B	Output
0	0	
0	1	
1	0	
1	1	

NAND gate


Input A	Input B	Output
0	0	
0	1	

1	0	
1	1	

(2)

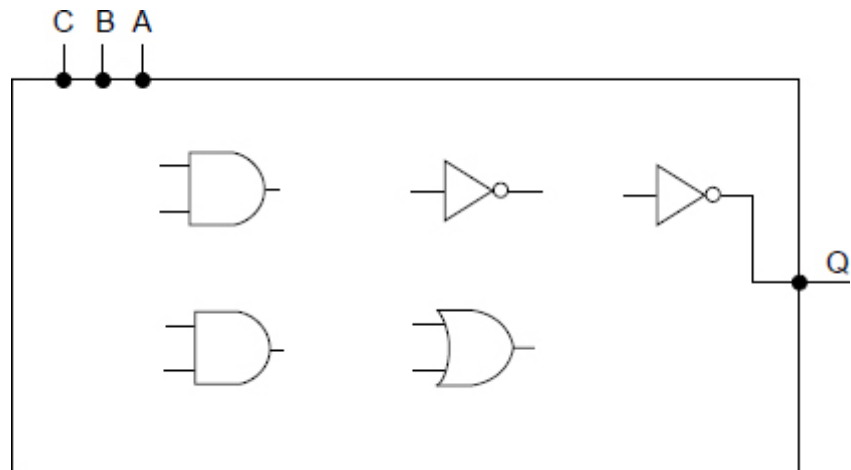- (b) Represent the following Boolean equation as a logic circuit by completing the diagram below.

$$Q = \overline{\overline{A \cdot B} + B \cdot C}$$



(5)

- (c) Simplify the following expression.

$$\overline{\overline{A} + \overline{B}} + B \cdot \overline{A}$$

Show each stage of your working.

(2)

**EXAM PAPERS PRACTICE**

Final answer \_\_\_\_\_

(1)

(Total 10 marks)

### Q6.

- (a) State the names of the logic gates represented by each of the three truth tables below.

Input A	Input B	Output
0	0	0
0	1	0

Logic gate name \_\_\_\_\_

1	0	0
1	1	1

Input A	Input B	Output
0	0	1
0	1	0
1	0	0
1	1	0

Logic gate name \_\_\_\_\_

Input A	Input B	Output
0	0	0
0	1	1
1	0	1
1	1	0

Logic gate name \_\_\_\_\_

(3)

(b) Simplify the following Boolean expressions.

(i)  $B \cdot (A + \bar{A})$

\_\_\_\_\_

EXAM PAPERS PRACTICE

(1)

(ii)  $A \cdot B + B$

\_\_\_\_\_

\_\_\_\_\_

(1)

(iii)  $\bar{B} \cdot (\bar{A} + \bar{B})$

\_\_\_\_\_



\_\_\_\_\_

(2)

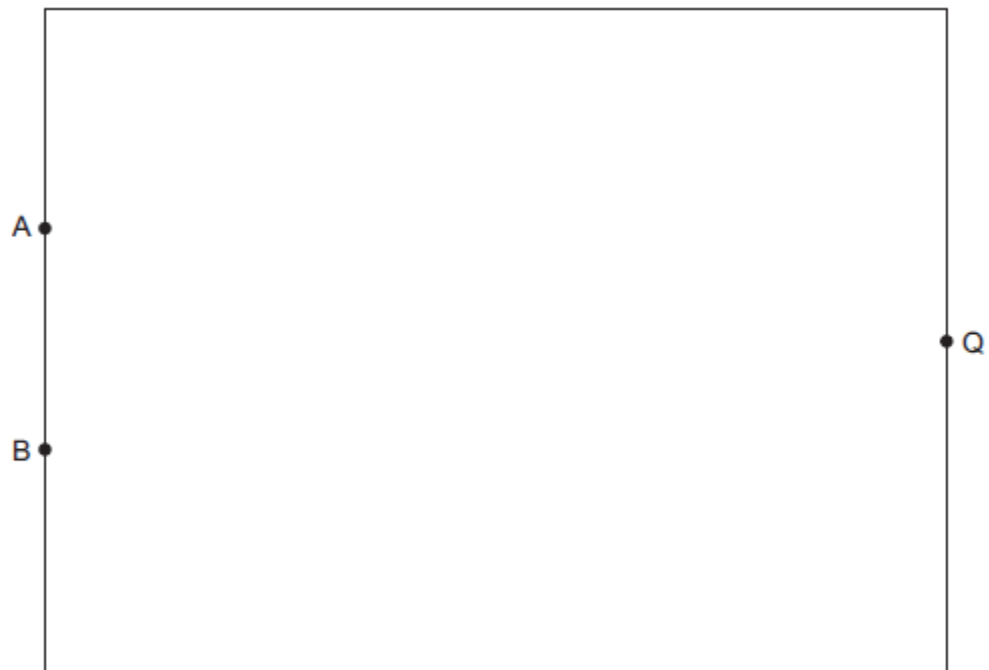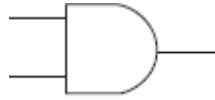(c) Draw a logic circuit for the following Boolean expression:

$$Q = (A \oplus B) \cdot B$$



You will need to make use of the symbols below when drawing your logic circuit.



(2)  
(Total 9 marks)

**Q7.**

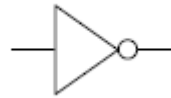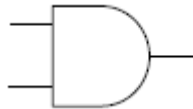- (a) Represent the Boolean equation  $Q = \overline{A} \cdot \overline{B}$  as a logic circuit by drawing a diagram using **only** the following symbols:



AND

NOT



(3)

- (b) Use the following truth tables to demonstrate that  $A + B = \overline{\overline{A} \cdot \overline{B}}$

A	B	A + B	A	B				$\overline{\overline{A} \cdot \overline{B}}$
0	0		0	0				
0	1		0	1				
1	0		1	0				
1	1		1	1				

(4)

- (c) What is the name commonly associated with the statement  $A + B = \overline{\overline{A} \cdot \overline{B}}$  ?

EXAM PAPERS PRACTICE

(1)

- (d) Simplify the Boolean expression below.

$$A.B.\overline{C} + A.\overline{C}$$

Show each stage of your workin.

(2)

Final answer \_\_\_\_\_

(1)

(Total 11 marks)

**Q8.**

- (a) Complete the truth tables for the following logic gates.

AND Gate		
Input X	Input Y	Input Q
0	0	
0	1	
1	0	
1	1	

XOR Gate		
Output X	Input Y	Output Q
0	0	
0	1	
1	0	
1	1	

(2)

- (b) A line-following robot has three sensors. It moves along a black line on a white background whilst the following conditions are met:

- the ultrasonic sensor U does not detect any obstacle
- either, but not both, of the infrared sensors L and R are on the black line.

Sensor U returns 1 if it detects an obstacle and 0 if the path is clear.

Sensors L and R each return 1 if they detect black and 0 if they detect white.

A logic circuit will process the input from the sensors and produce an output M.


M should be 1 if the robot is to move and 0 if the robot should stop.

- (i) Represent the output M as a Boolean expression.


M = \_\_\_\_\_

(3)

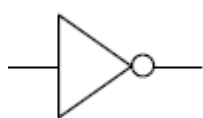- (ii) The following symbols are used to represent logic gates:




NOT

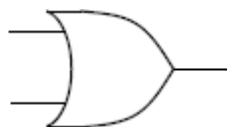


OR




AND

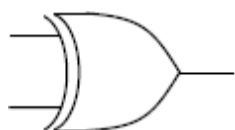

XOR

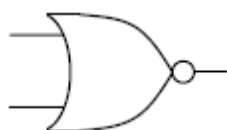

NOR

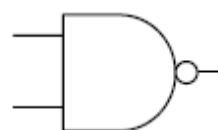

NAND

Using a combination of any of the above logic gates draw a logic circuit for this system in the box below. You will **not** need to use all of the different types of logic gates.



(3)

- (c) Apply De Morgan's Law(s) to the following expression and simplify the result.

$$Q = \overline{\overline{A} + (\overline{B} \cdot \overline{A})}$$

Show the stages of your working.

---

---

---

---

---

(2)

Final answer


EXAM PAPERS PRACTICE

(1)

(Total 11 marks)

**Q9.**

The diagram below shows a logic circuit.

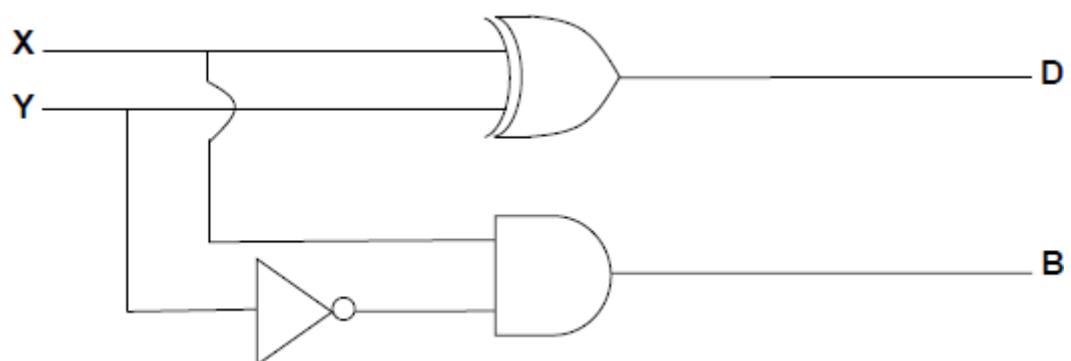

- (a) Write a Boolean expression for **D**.

---


(1)

- (b) Write a Boolean expression for **B**.

\_\_\_\_\_

(1)

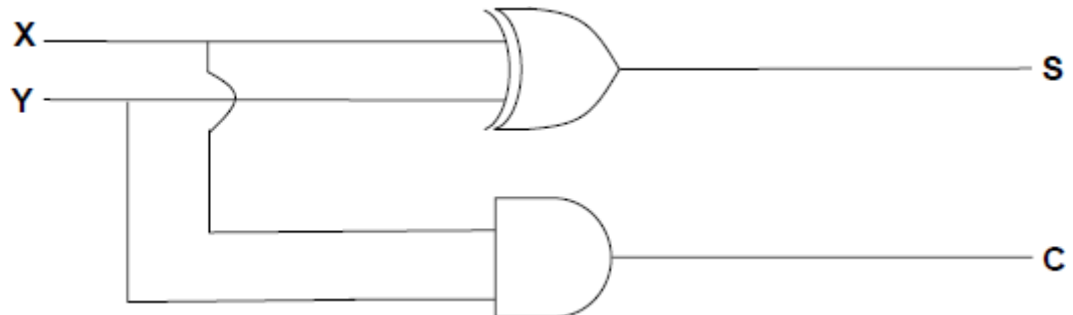- (c) The diagram below shows a different logic circuit.



- (i) Complete the truth table below for the logic circuit in the diagram above.

Inputs		Outputs	
X	Y	C	S
0	0		
0	1		
1	0		
1	1		

(2)

EXAM PAPERS PRACTICE

- (ii) What arithmetic function does the logic circuit in the diagram above perform?

\_\_\_\_\_

(1)

- (d) **Without** using a truth table, simplify the Boolean expression below.

$$(X + Y) \cdot (X + \bar{Y})$$

Show the stages of your working.

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

---

---

---

---

---

---

(3)

Final answer \_\_\_\_\_

(1)

(Total 9 marks)

**Q10.**


- (a) Complete the truth tables for the following logic gates.

NAND Gate		
Input X	Input Y	Output Q
0	0	
0	1	
1	0	
1	1	

NOR Gate		
Input X	Input Y	Output Q
0	0	
0	1	
1	0	
1	1	

(2)

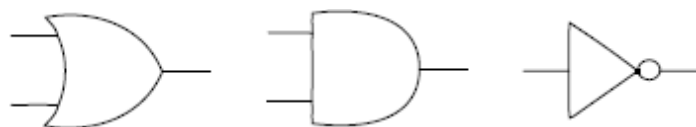- (b) Represent the Boolean equation  $Z = \bar{A} \cdot \bar{B} + C$  in the form of a logic circuit by drawing a diagram using the following symbols.



OR

AND

NOT



(3)

- (c) Simplify the Boolean expression below.

$$\overline{(A \cdot B)} + \overline{(A \cdot \bar{B})}$$

Show each stage of your working.

---



---



---



---

EXAM PAPERS PRACTICE

(3)

Final answer \_\_\_\_\_

(1)

(Total 9 marks)

### Q11.

Write the following Boolean expressions in their simplest forms.

(a)  $\overline{(\bar{A} \cdot \bar{B})}$

---

(1)

(b)  $B + B \cdot \bar{C}$

---

(1)

(c)  $A \cdot B + A \cdot \bar{B}$

---

(1)

(d)  $A \cdot (B+1)$

(1)

(Total 4 marks)


**Q12.**

(a) Complete the truth tables for the following logic gates.

OR Gate			XOR Gate		
Input A	Input B	Output Q	Input A	Input B	Output Q
0	0		0	0	
0	1		0	1	
1	0		1	0	
1	1		1	1	

(2)

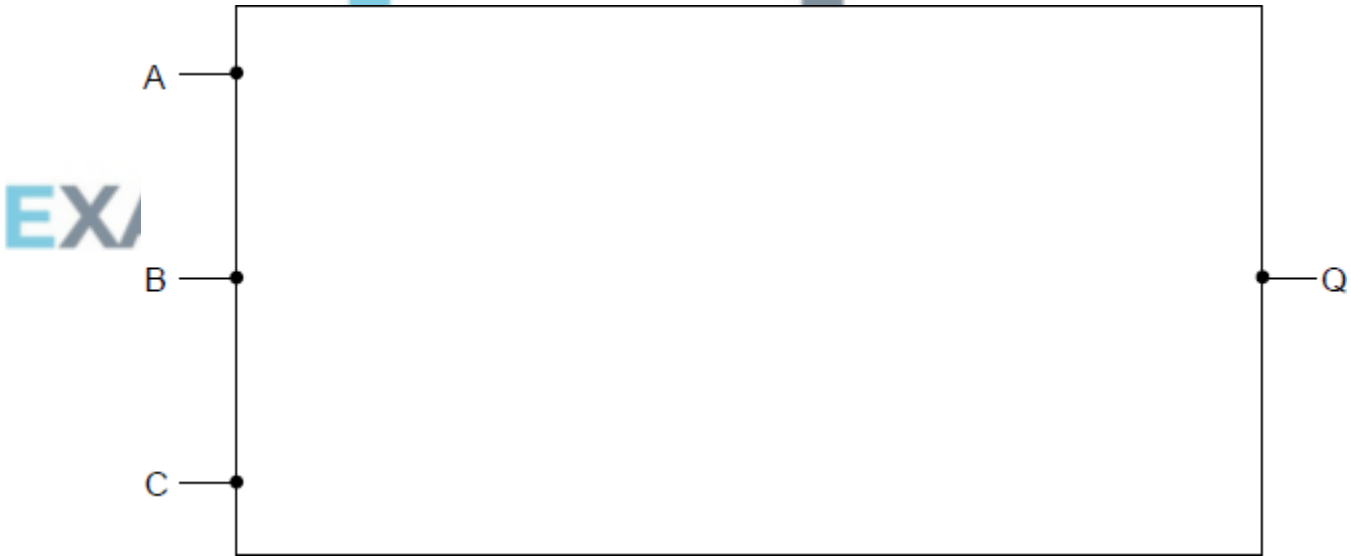(b) Represent the Boolean equation  $Q = A + B \cdot \overline{C}$  as a logic circuit by drawing a diagram of it.



(3)

(c) Simplify the Boolean expression:

$$B \cdot (A + \overline{B})$$

Show your working.

(3)  
(Total 8 marks)

**Q13.**

Simplify the Boolean expression:

$$\overline{A \cdot B} + A$$

Show your working.

(Total 3 marks)

**Q14.**

(a) Look at the truth table below.

Input A	Input B	Output Q
0	0	1
0	1	0
1	0	0
1	1	0

What logic gate does the table represent?

(1)

(b) An interior light in a two-door car is controlled by two switches that the driver can turn on or off and two sensors, one per door.

The switches are named A and B.

The door sensors are named C and D.


The interior light is named L.

If a door is open the output of its sensor is on.


If a door is closed the output of its sensor is off.

- If both switches A and B are off then the light L is always off.
- If switch A is on the light L is always on.
- If switch B is on and switch A is off then:
  - the light L turns on if one or more of the car doors is opened
  - the light L turns off if both of the doors are closed.

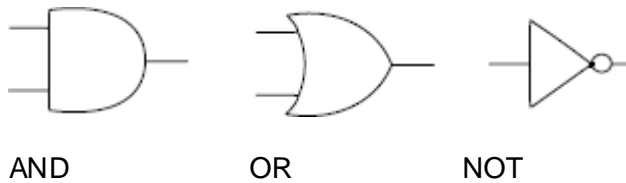The following symbols are used to represent logic gates:



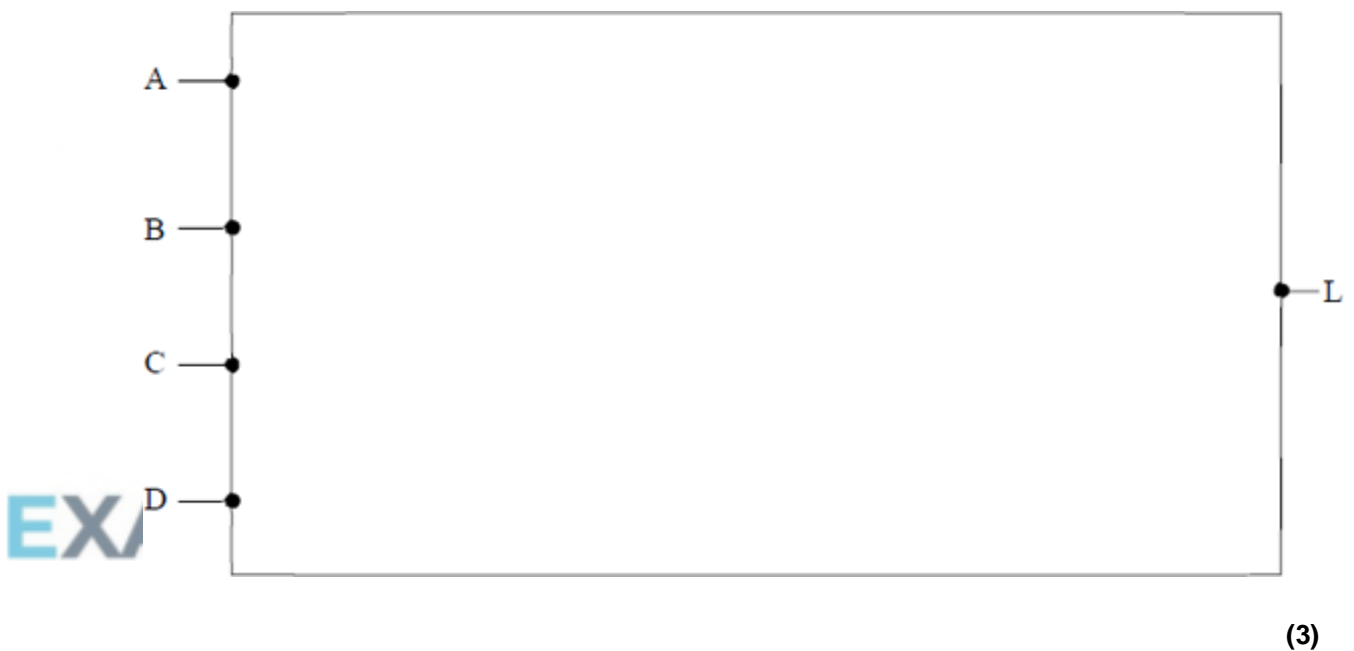- (i) Using only AND, OR and NOT gates draw a logic circuit for this system in the box below. You may not need to use all three types of gate.



- (ii) Write a Boolean expression to represent the logic of the interior light system.

\_\_\_\_\_ (1)

- (c) Simplify the Boolean expression below, showing your working.

$$\overline{\overline{A} + \overline{B}} + B \cdot \overline{A}$$

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

---

---

---

---

---

---

(3)  
(Total 8 marks)

**Q15.**

- (a) Complete the truth tables for the following logic gates.

**OR gate**

Input A	Input B	Output
0	0	
0	1	
1	0	
1	1	

**AND gate**

Input A	Input B	Output
0	0	
0	1	
1	0	
1	1	

(2)

- (b) (i) A single output Q is produced from three inputs A, B and C. Output Q is required to be 1 only if inputs A and B are 1, or input C is 1 and input B is 0.


Express this as a Boolean equation.

EXAM PAPERS PRACTICE

Q = \_\_\_\_\_

(2)

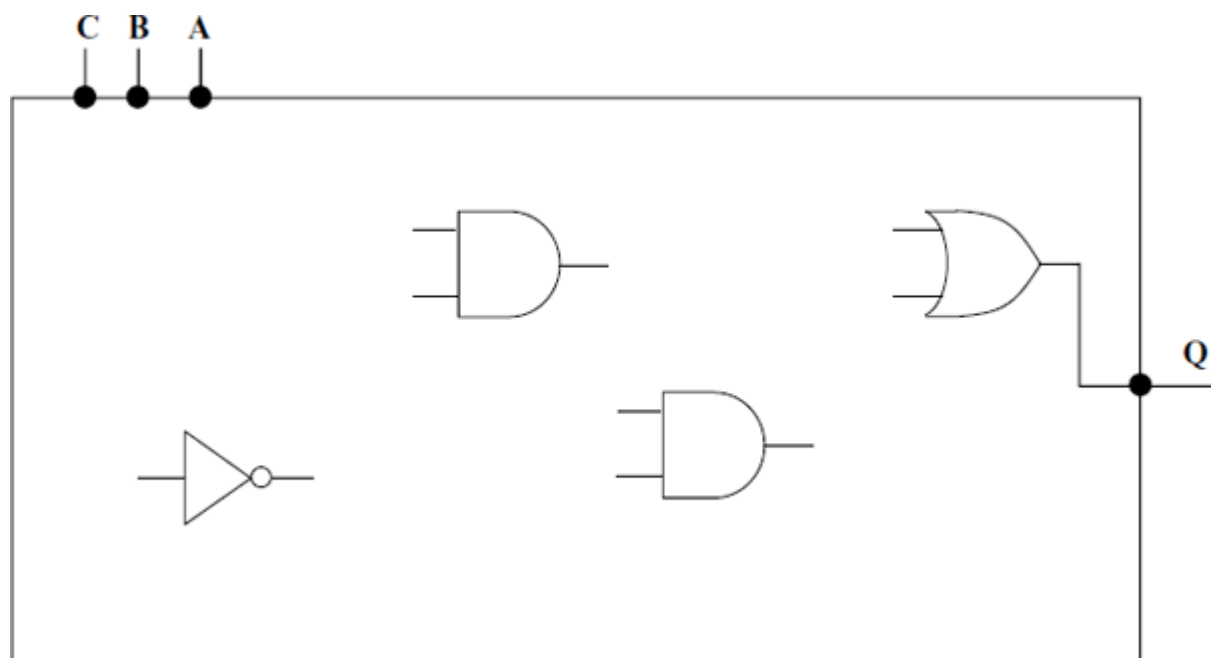- (ii) Represent this Boolean equation diagrammatically by completing the logic gate diagram below.



(4)  
(Total 8 marks)



**EXAM PAPERS PRACTICE**