

Capacitor Charge & Discharge

Mark Scheme

Level	A Level
Subject	Physics
Exam Board	AQA
Paper Type	Multiple Choice

Time Allowed : 30min

1. C
2. C
3. A
4. D
5. C
6. D
7. D
8. B
9. A
10. D
11. D
12. B
13. B
14. B
15. D
16. D
17. C
18. A
19. A
20. A